

# Bishop Bronescombe C of E Primary School



Topic: Electricity (Y6)

Year 5/6

Strand: Physics

## What your child should already know:

- identify common appliances that run on electricity.
- construct a simple series electrical circuit, identifying and naming its basic parts, including cells, wires, bulbs, switches and buzzers .
- identify whether or not a lamp will light in a simple series circuit, based on whether or not the lamp is part of a complete loop with a battery.
- recognise that a switch opens and closes a circuit and associate this with whether or not a lamp lights in a simple series circuit.
- recognise some common conductors and insulators, and associate metals with being good conductors.

## By the end of the unit, your child should be able to:

- associate the brightness of a lamp or the volume of a buzzer with the number and voltage of cells used in the circuit.
- compare and give reasons for variations in how components function, including the brightness of bulbs, the loudness of buzzers and the on/off position of switches.
- use recognised symbols when representing a simple circuit in a diagram.


## Key Vocabulary

| Word                | Meaning  |
|---------------------|--|
| <b>circuit</b>      | A path that an electrical <b>current</b> can flow around   |
| <b>symbol</b>       | A visual picture that stands for something else.   |
| <b>cell/battery</b> | A device that stores energy as a chemical until it is needed. A <b>cell</b> is a single unit. A <b>battery</b> is a collection of cells. |
| <b>current</b>      | The flow of <b>electrons</b> , measured in <b>amps</b> .   |
| <b>amps</b>         | How electric <b>current</b> is measured.   |
| <b>voltage</b>      | The force that makes the electric current move through the wires. The greater the <b>voltage</b> , the more current will flow .          |
| <b>resistance</b>   | The difficulty that the electric <b>current</b> has when flowing around a <b>circuit</b> .   |
| <b>electrons</b>    | Very small particles that travel around an electrical <b>circuit</b> .   |



## Key Knowledge
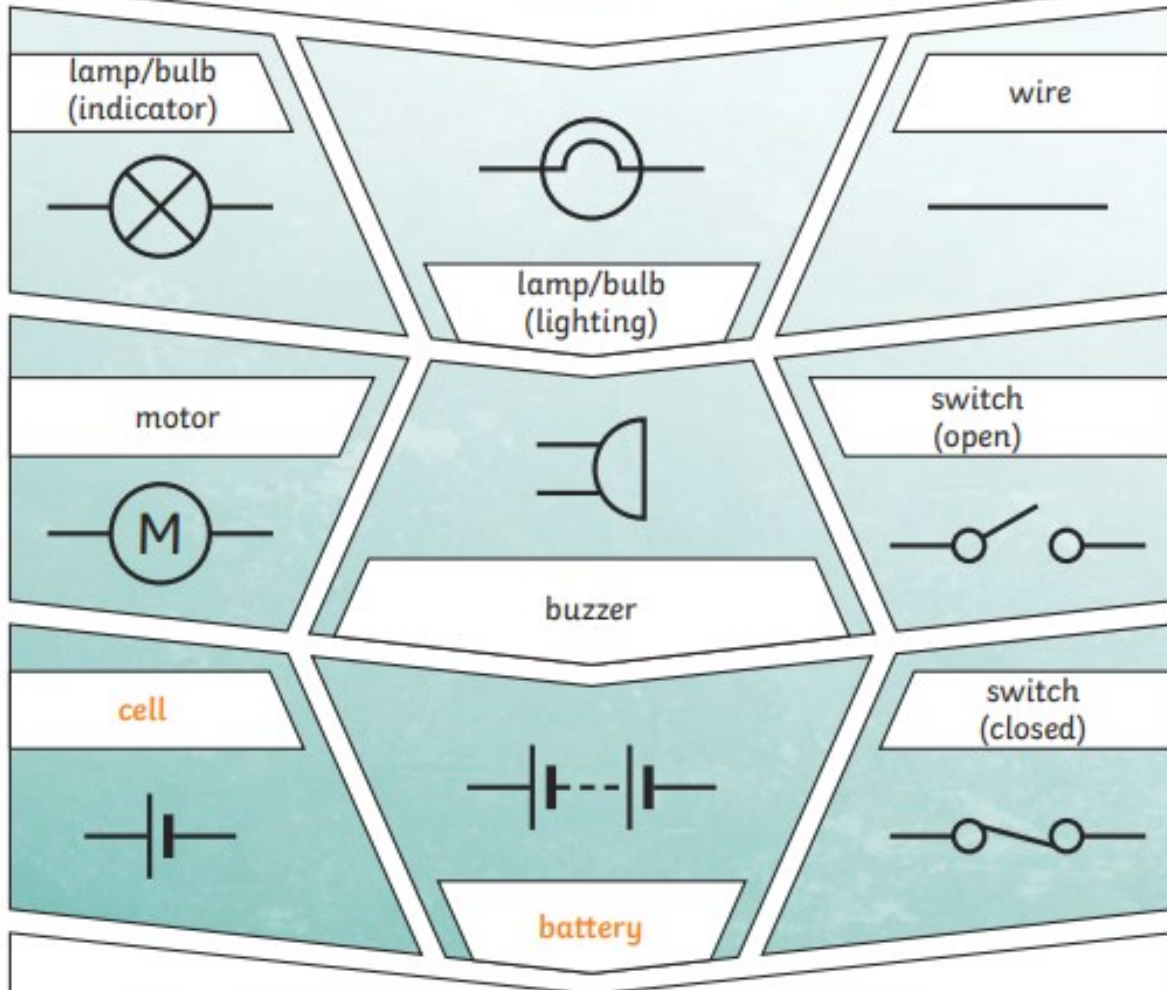
### Components of a **Circuit** and Their **Symbols**



These **symbols** can be used to create electrical **circuit** diagrams.

### What will make a bulb brighter or a buzzer louder?

- more batteries or a higher voltage create more power to flow through the circuit.
- Shortening the wires means the electrons have less resistance to flow through.

### What will make a bulb dimmer or a buzzer quieter?

- fewer batteries or a lower voltage give less power to the circuit.
- More buzzers or bulbs mean the power is shared by more components.
- Lengthening the wires means the electrons have to travel through more resistance.



### Series Circuit

A circuit that has only one route for the current to take. If more bulbs or buzzers are added, the power has to be shared and so they will be dimmer or quieter. If just one part of the series circuit breaks, the circuit is broken and the flow of current stops.